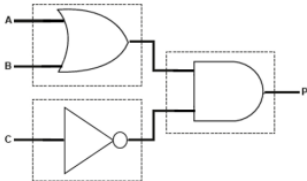



2.4 – Boolean Logic – Past Exam Questions – Solutions


2022

2	(a)	(i)	<ul style="list-style-type: none"> A OR B NOT C AND gate 	3 (AO2 1b)	<p>1 mark per gate. Correct symbols must be used.</p> <p>NOT gate must have circle for inversion, OR and AND must <u>not</u> have a circle.</p> <p>Mark the shape of each gate, not the name written if given. Ignore any writing / notes.</p> <p>Lines do not have to be drawn or joined up, but if they are, gates must have the correct number of inputs/outputs. Penalise once then FT.</p>
2	(a)	(ii)	<ul style="list-style-type: none"> To show all possible inputs (to the logic circuit)... ...and the associated/dependent output (for each input) 	2 (AO1 1b)	<p>For 2nd BP, must be clear that the output is linked to the input values given.</p> <p>"All possible combinations of inputs and outputs" gains the first mark (all possible inputs) but not the second.</p> <p>"The output for each possible input" gains both marks</p>
2	(a)	(iii)	<ul style="list-style-type: none"> 8 // eight 	1 (AO2 1a)	<p>Accept other answers that equate to 8 (e.g. 2³)</p>

Sample Paper

1	a	<table><tr><th>A</th><th>B</th><th>P</th></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td>1</td></tr><tr><td></td><td></td><td>1</td></tr><tr><td></td><td></td><td></td></tr></table>	A	B	P						1			1				2 (AO1 1b)	1 mark for each correct answer in table 'True' or 'T' are also credit worthy.
	A	B	P																
		1																	
		1																	
	b		1 (AO1 1b)	Correct Answer Only															

2020

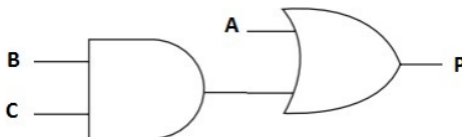4	f	i	<p>1 mark per bullet point</p> <ul style="list-style-type: none">• B AND C• OR gate with two inputs, one of which is A• ...correct connection of these two gates with no additional gates / connections	3 AO1 1b(3)	<p>Shape must be accurate</p> 															
4	f	ii	<p>1 mark per bullet point</p> <ul style="list-style-type: none">• Correct completion of A and B inputs as 1 1• 0 output for 01 input• 0 output for 10 input• 0 output for 11 input	4 AO1 1b(1) AO2 1b(3)	<p>CAO</p> <table><tr><th>A</th><th>B</th><th>P</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	P	0	0	1	0	1	0	1	0	0	1	1	0
A	B	P																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		

2019

5	(e)	1 mark per missing bit	4 AO2 1b (4)	Accept T / True															
<table><tr><th>A</th><th>B</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>					A	B	Q	0	0	0	0	1	1	1	0	1	1	1	1
A	B	Q																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

2018

3	(a)	(ii)	4	1 mark per row
</				

2014

7			4	No follow through on row 4.															
		<table> <tr> <th>A</th><th>b</th><th>NOT(a AND b)</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table> <p>1 mark for row two and three. For row 4, 1 mark for correctly identifying 1 1 as the inputs, and 1 mark for the correct output 0)</p>	A	b	NOT(a AND b)	0	0	1	0	1	1	1	0	1	1	1	0		
A	b	NOT(a AND b)																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	